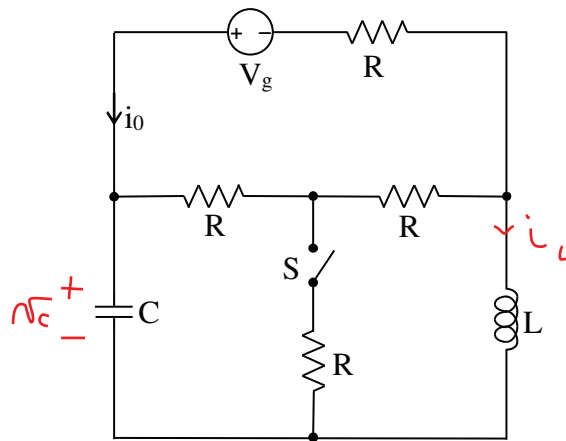


1) L'interruttore S chiude quando il circuito è a regime. Calcolare la corrente  $i_0(t)$ .

$$\left\langle \begin{aligned} i_0(t) &= 8e^{-12t} \cos(16t + \pi) + 24 \text{ A} \\ i_L(t) &= 4\sqrt{10}e^{-12t} \cos(16t - 0.322) - 12 \text{ A} = 12e^{-12t} \cos(16t) + 4e^{-12t} \sin(16t) - 12 \text{ A} \\ v_C(t) &= 4\sqrt{10}e^{-12t} \cos(16t + 1.249) + 36 \text{ V} = 4e^{-12t} \cos(16t) - 12e^{-12t} \sin(16t) + 36 \text{ V} \end{aligned} \right\rangle$$

$$R = 1 \Omega, C = 50 \text{ mF}, L = 50 \text{ mH}, V_g = 60 \text{ V}$$



2) Calcolare il campo magnetico  $H_0$  al traferro.

$$\langle H_0 = 1053 \text{ kA/m} \rangle$$

$$I = 10 \text{ A}, N_1 = 100, N_2 = 50, N_3 = 200, S = 1 \text{ cm}^2, a = 30 \text{ cm}, b = 40 \text{ cm}, \delta = 1 \text{ mm}, \mu_r = 10^3$$

